


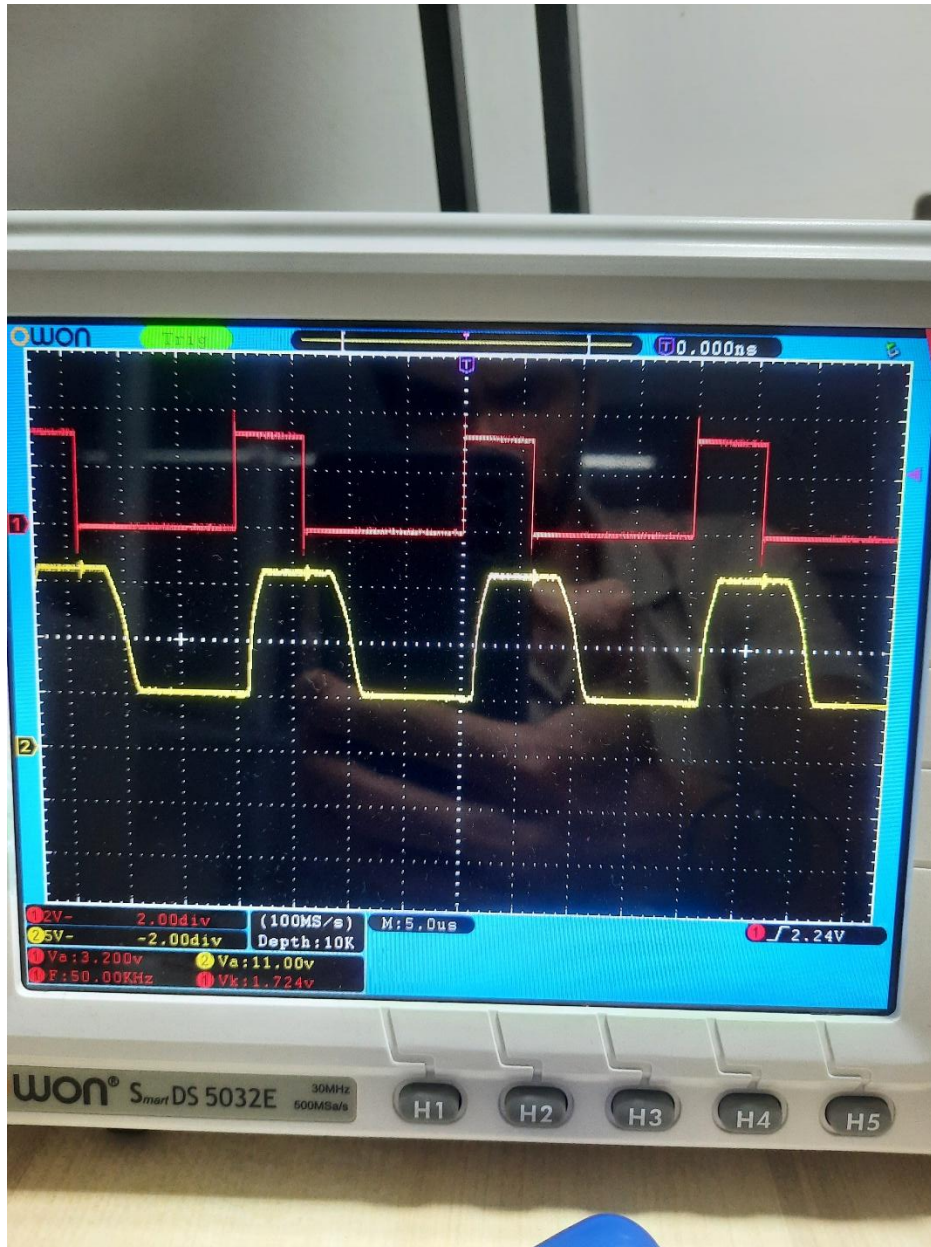



VFD Control System: Development Portfolio

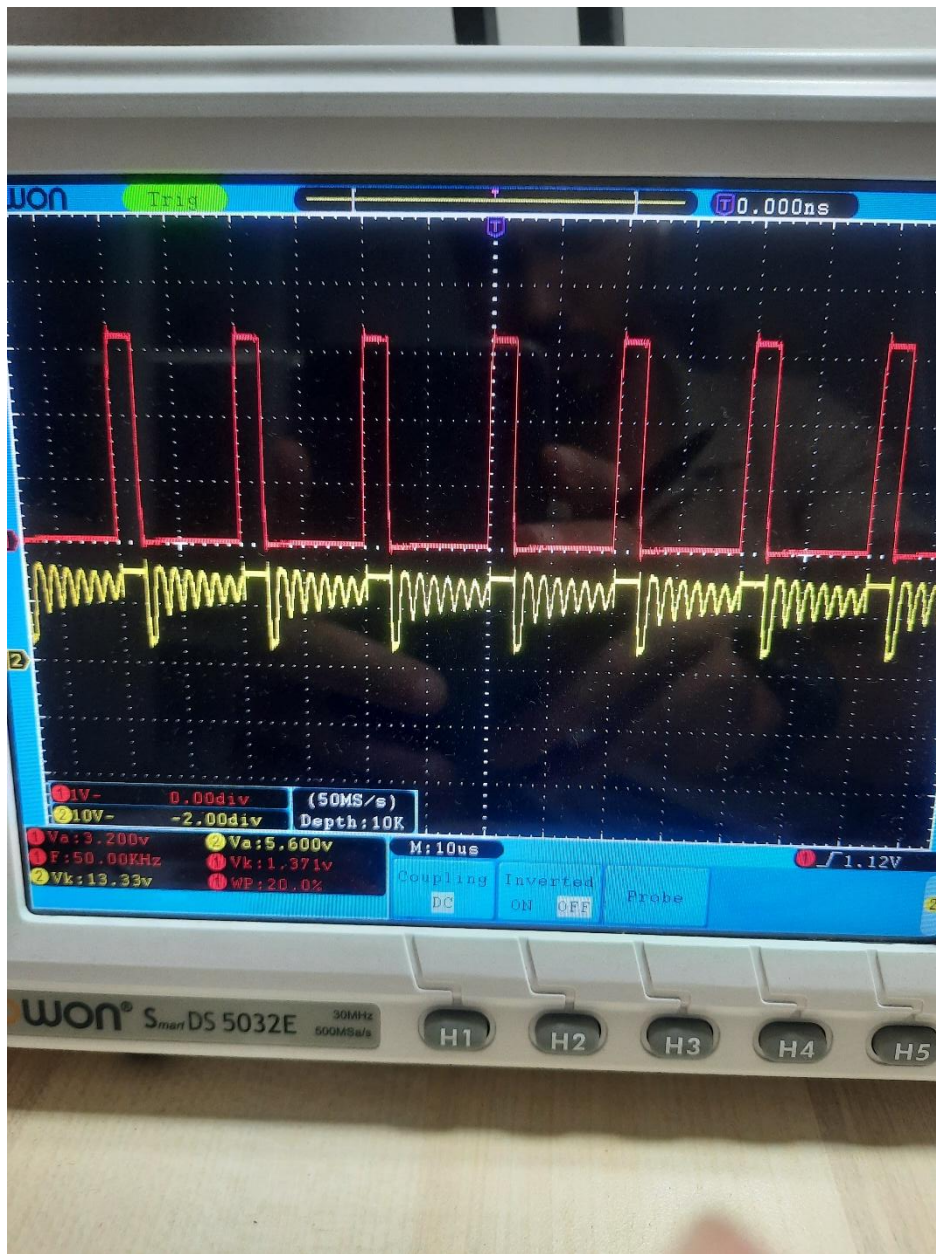

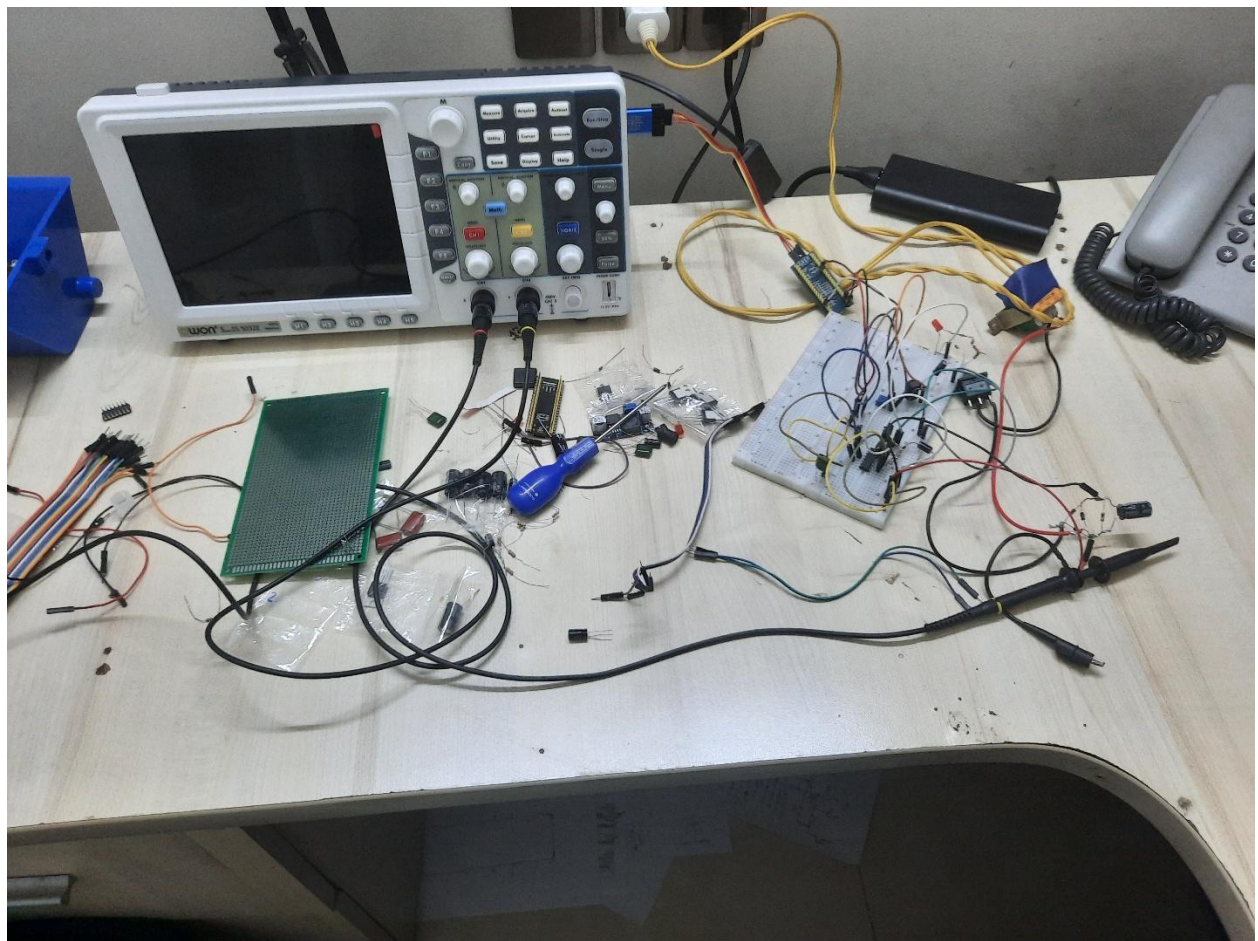

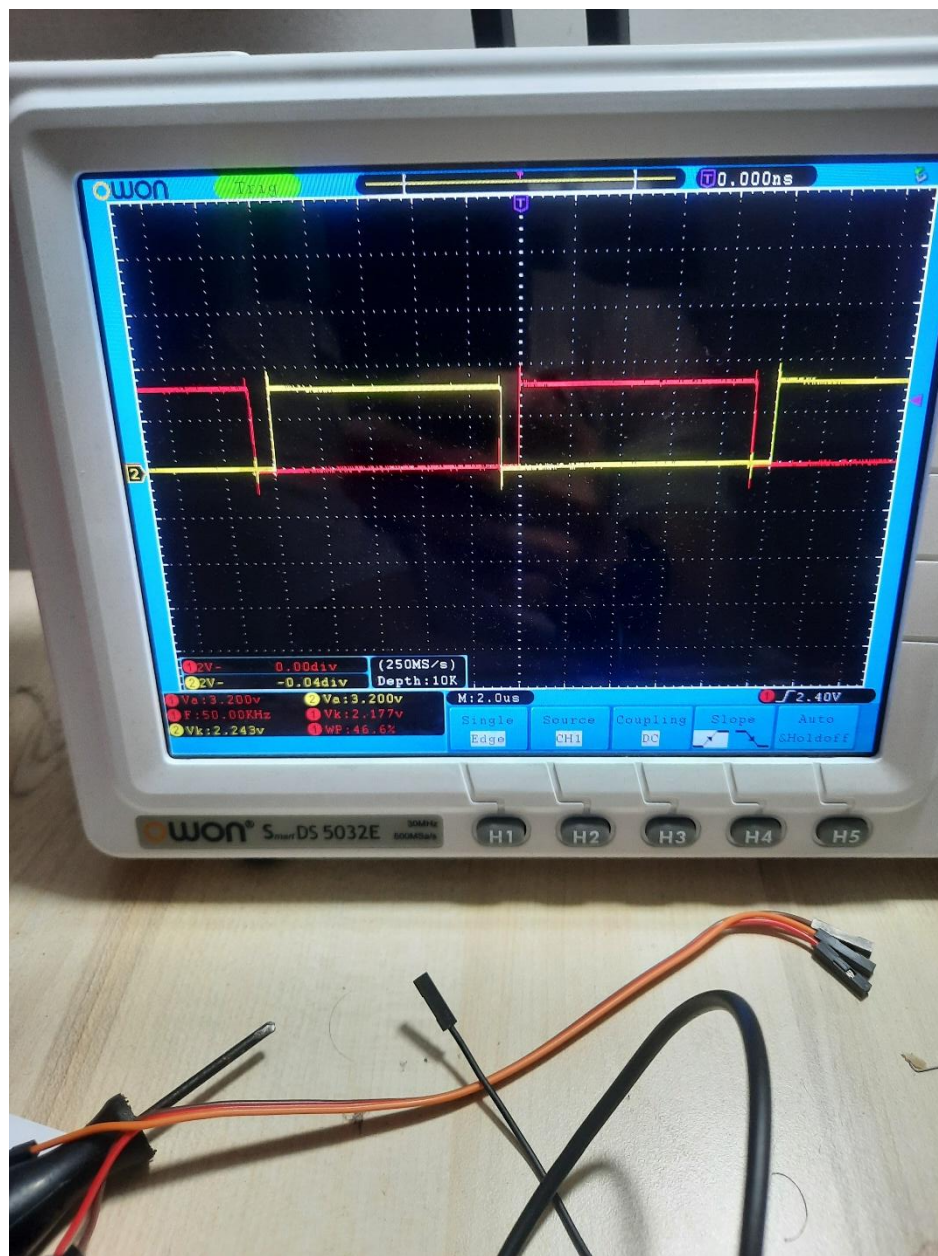



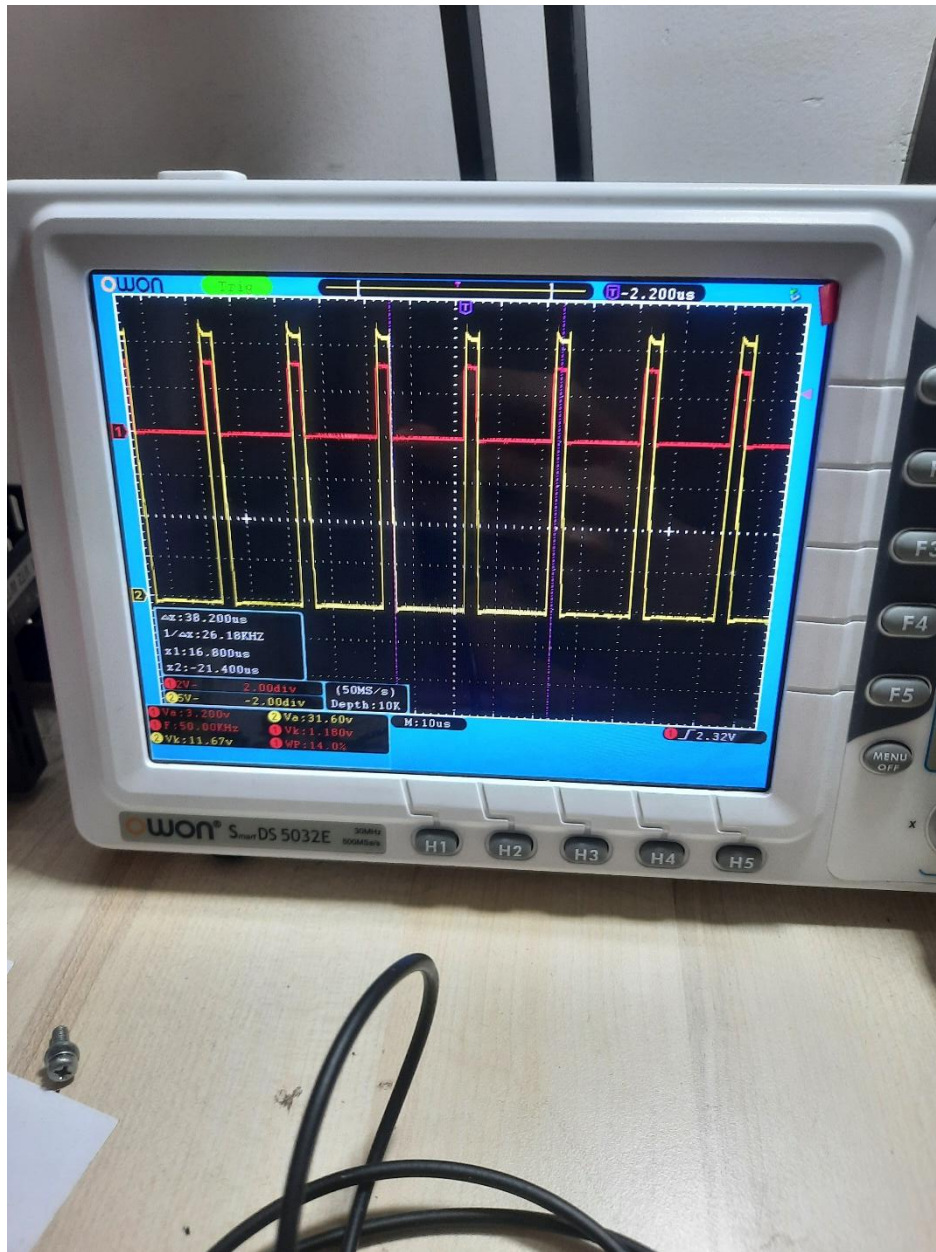

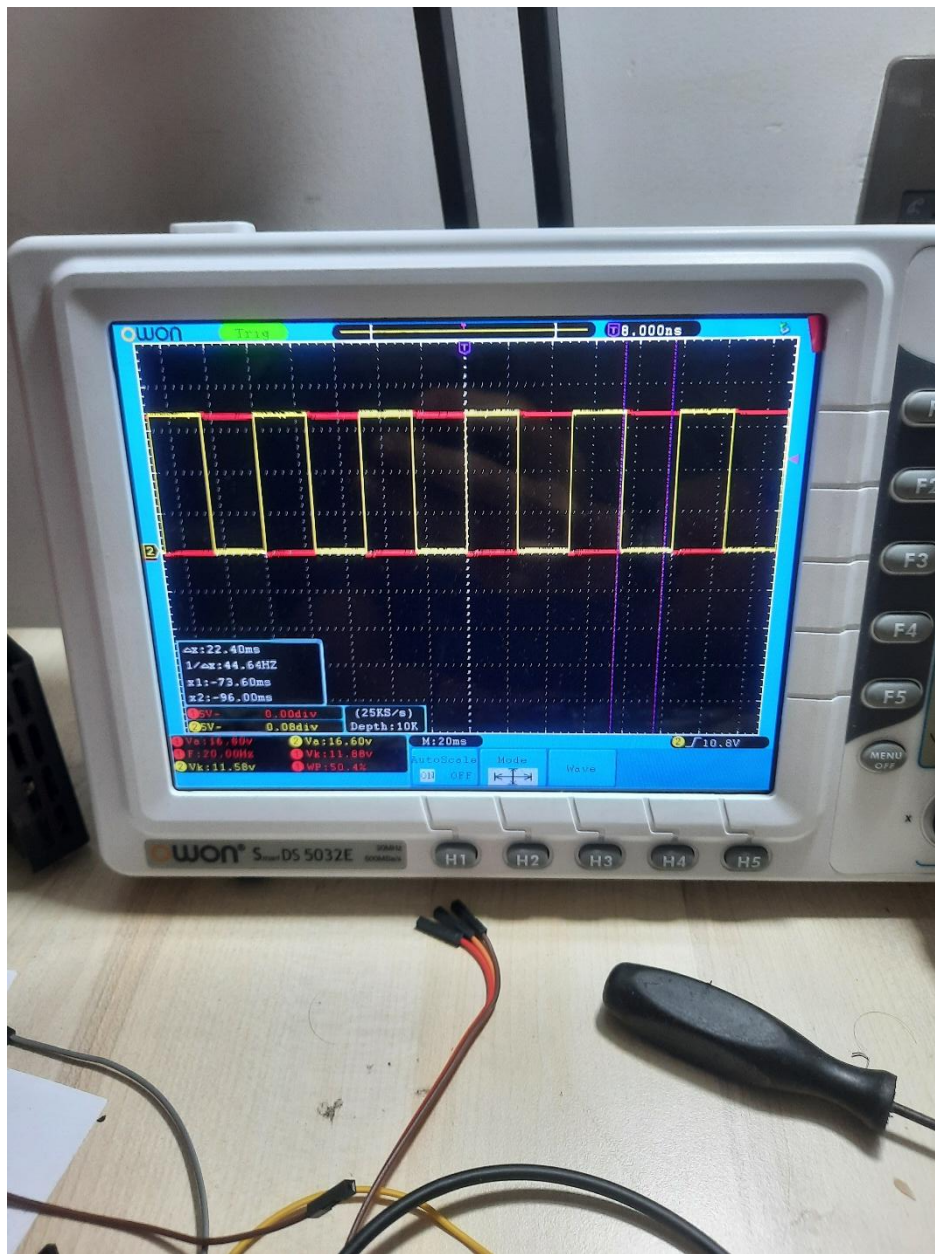
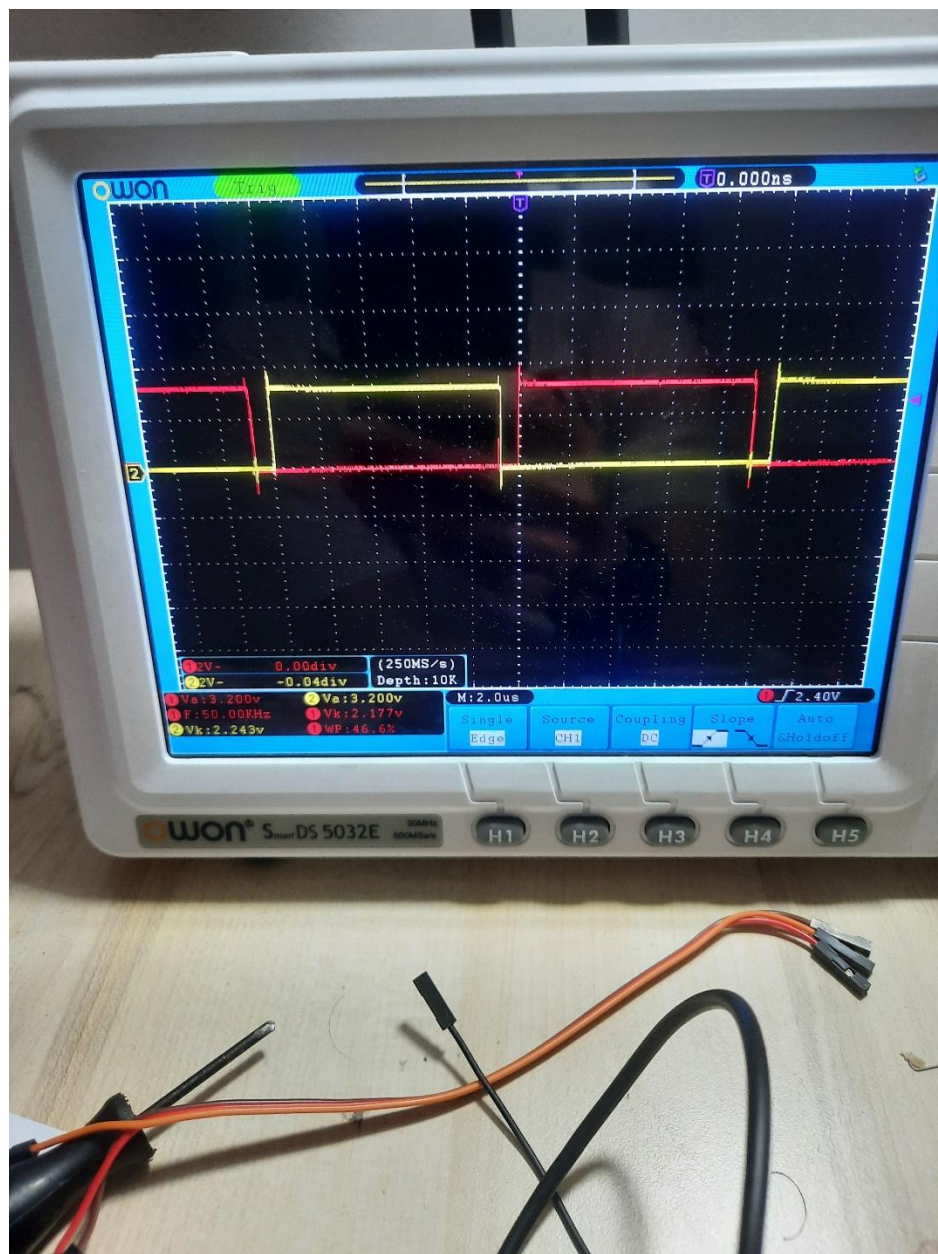
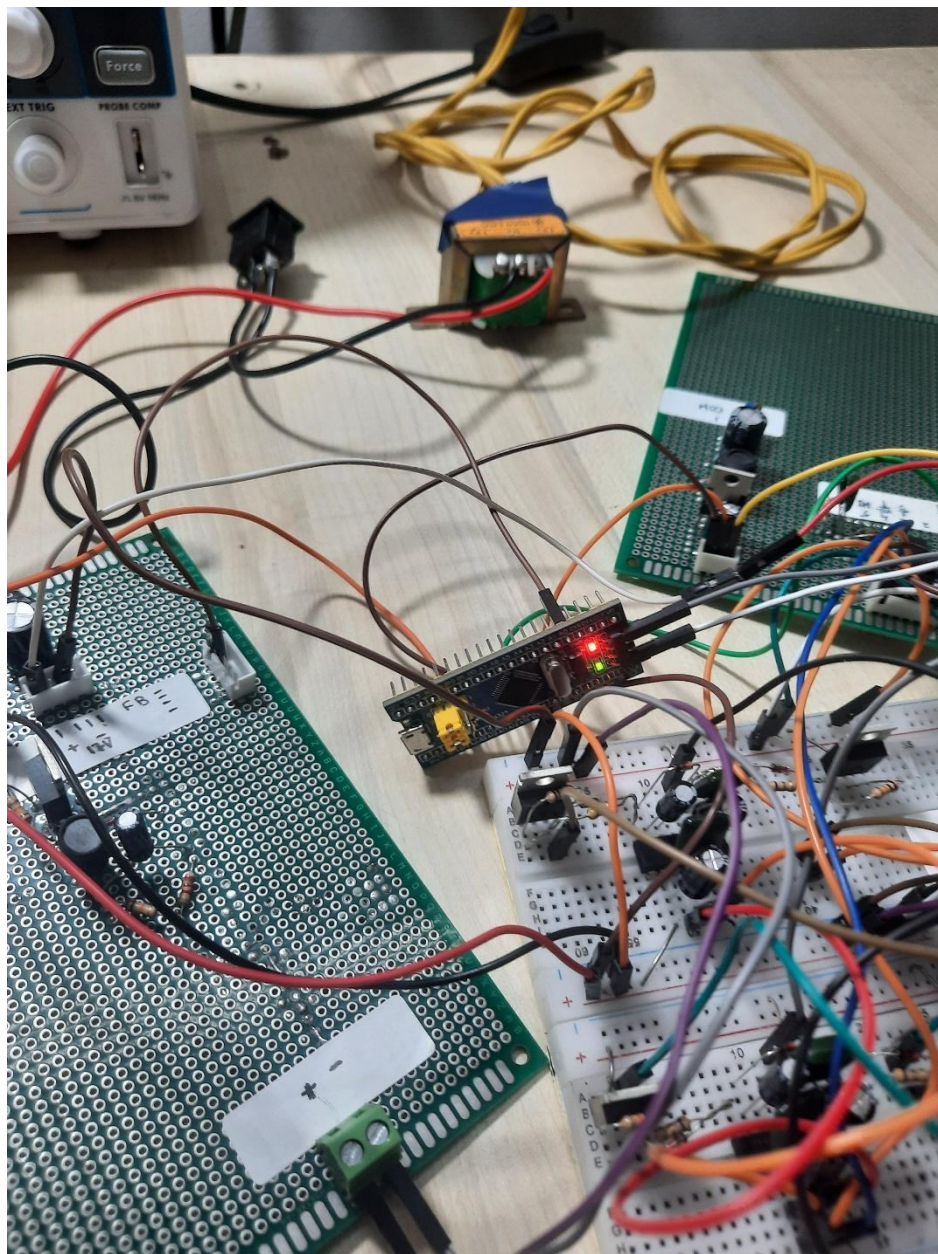
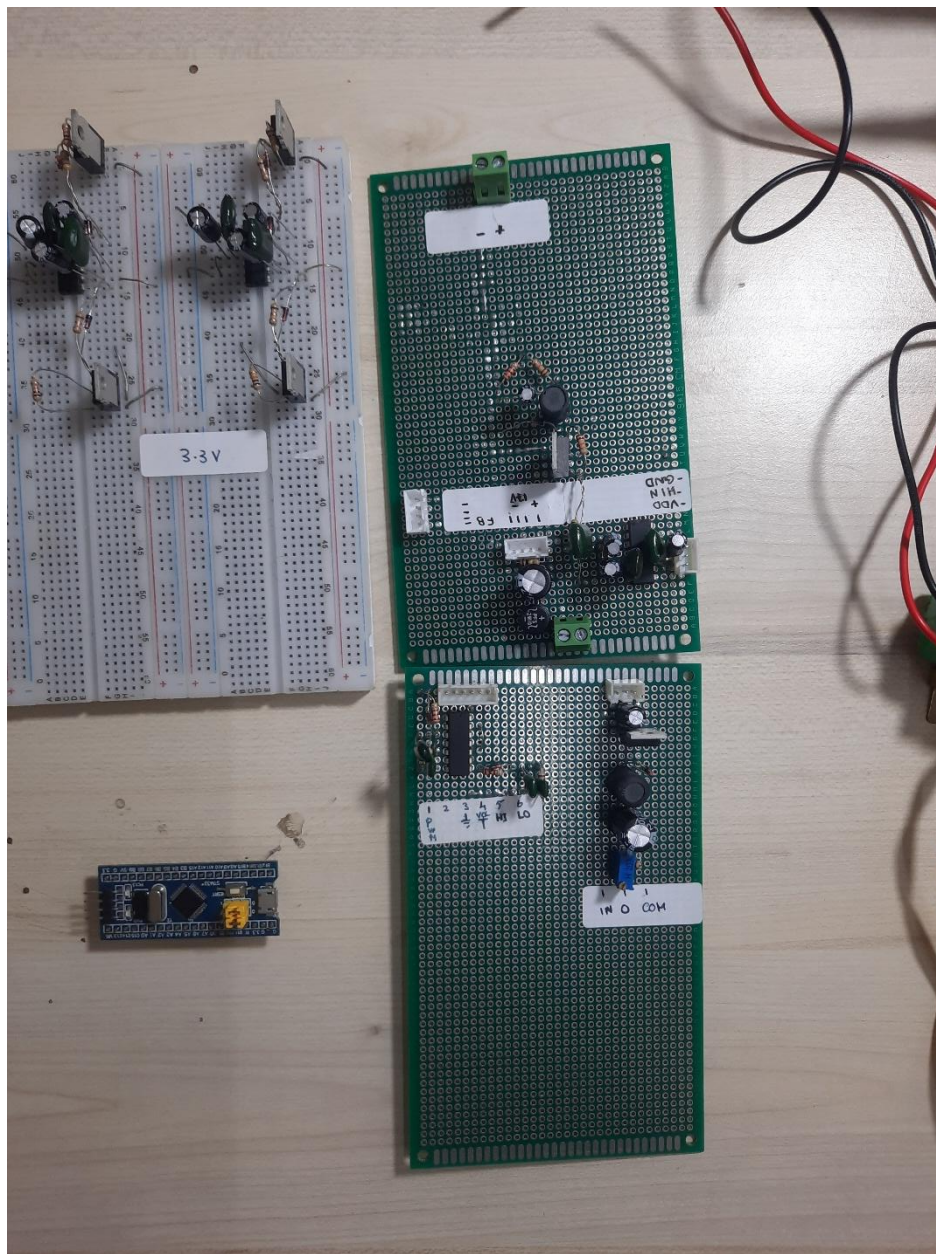


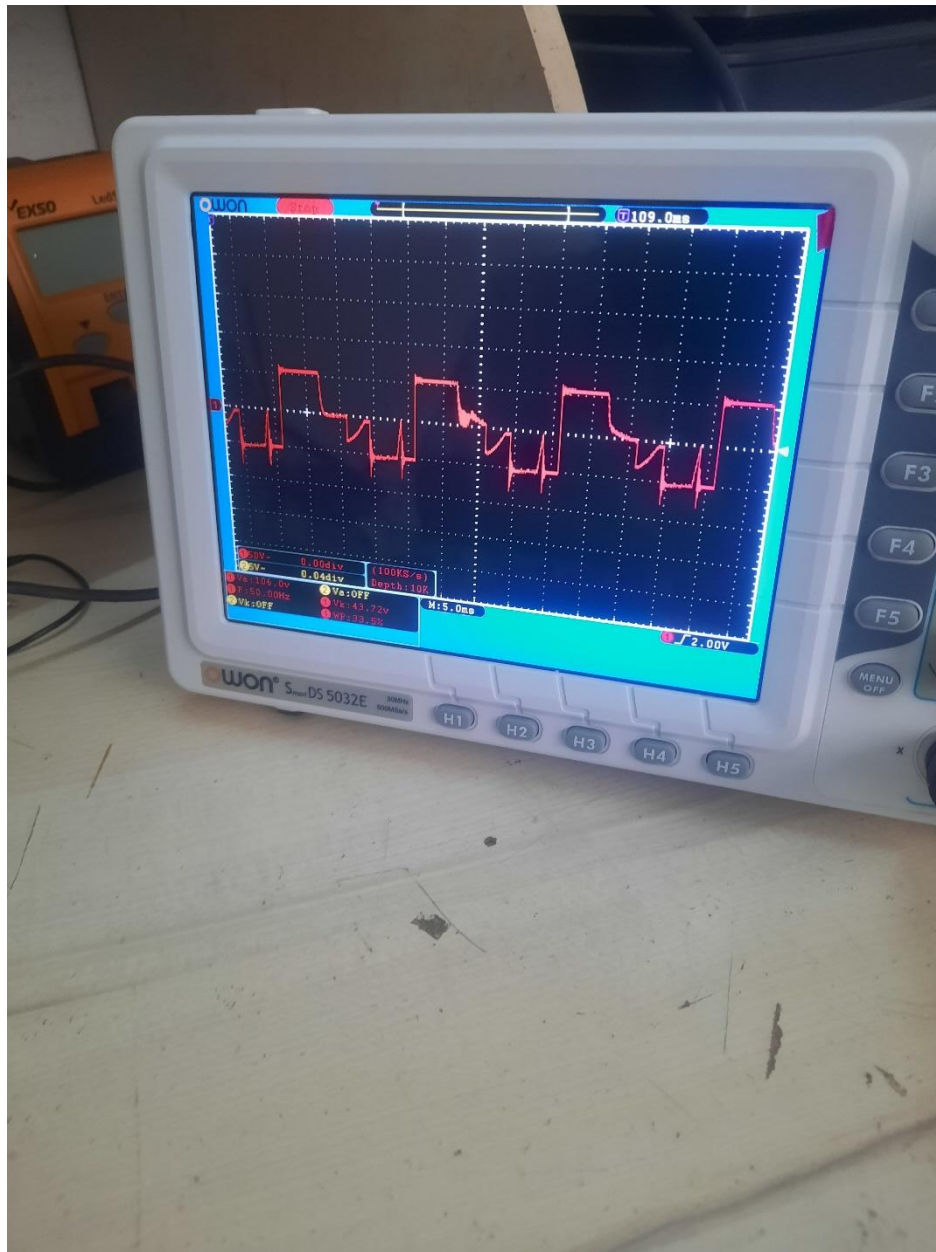
Figure 1 Deadtime generation circuit testing

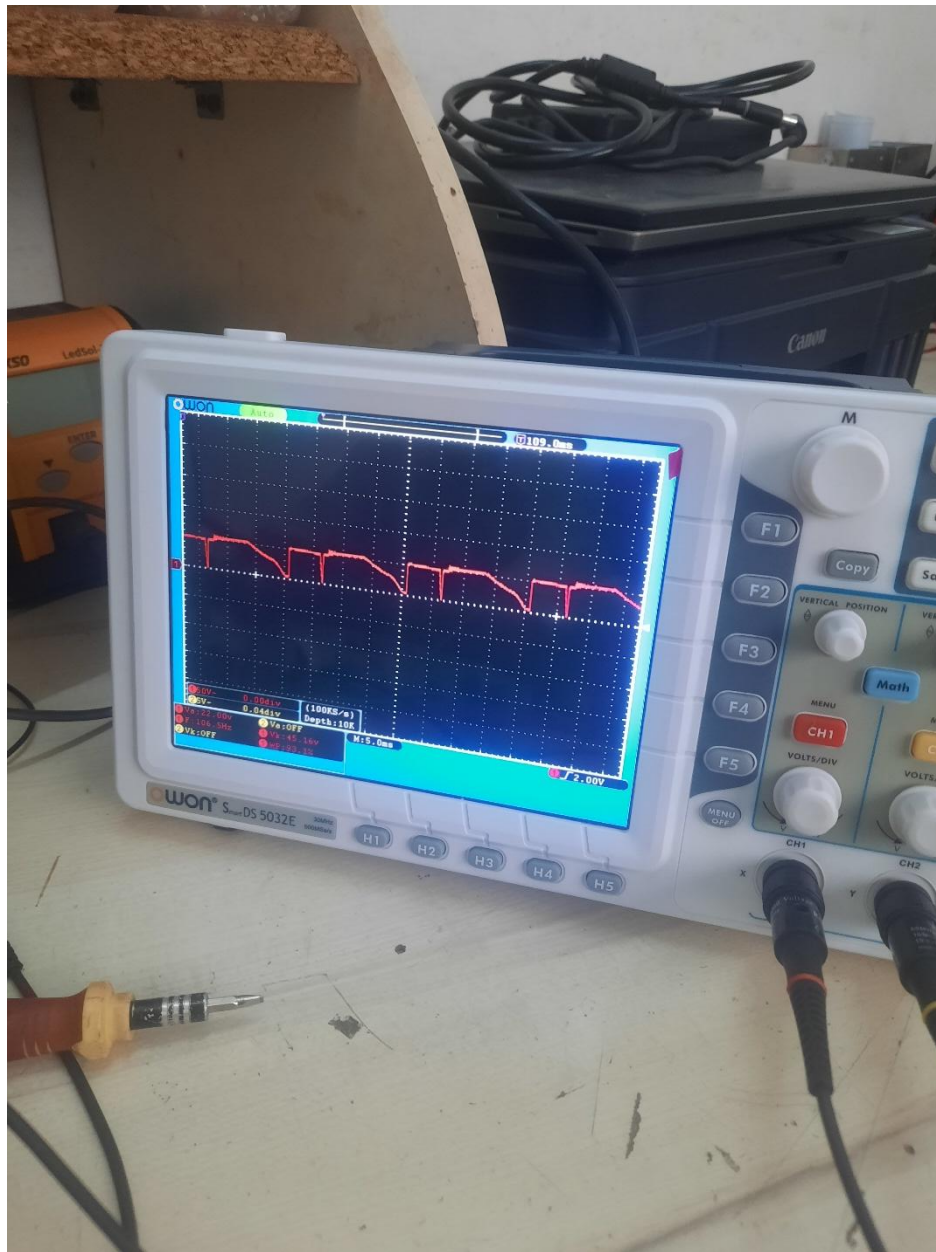













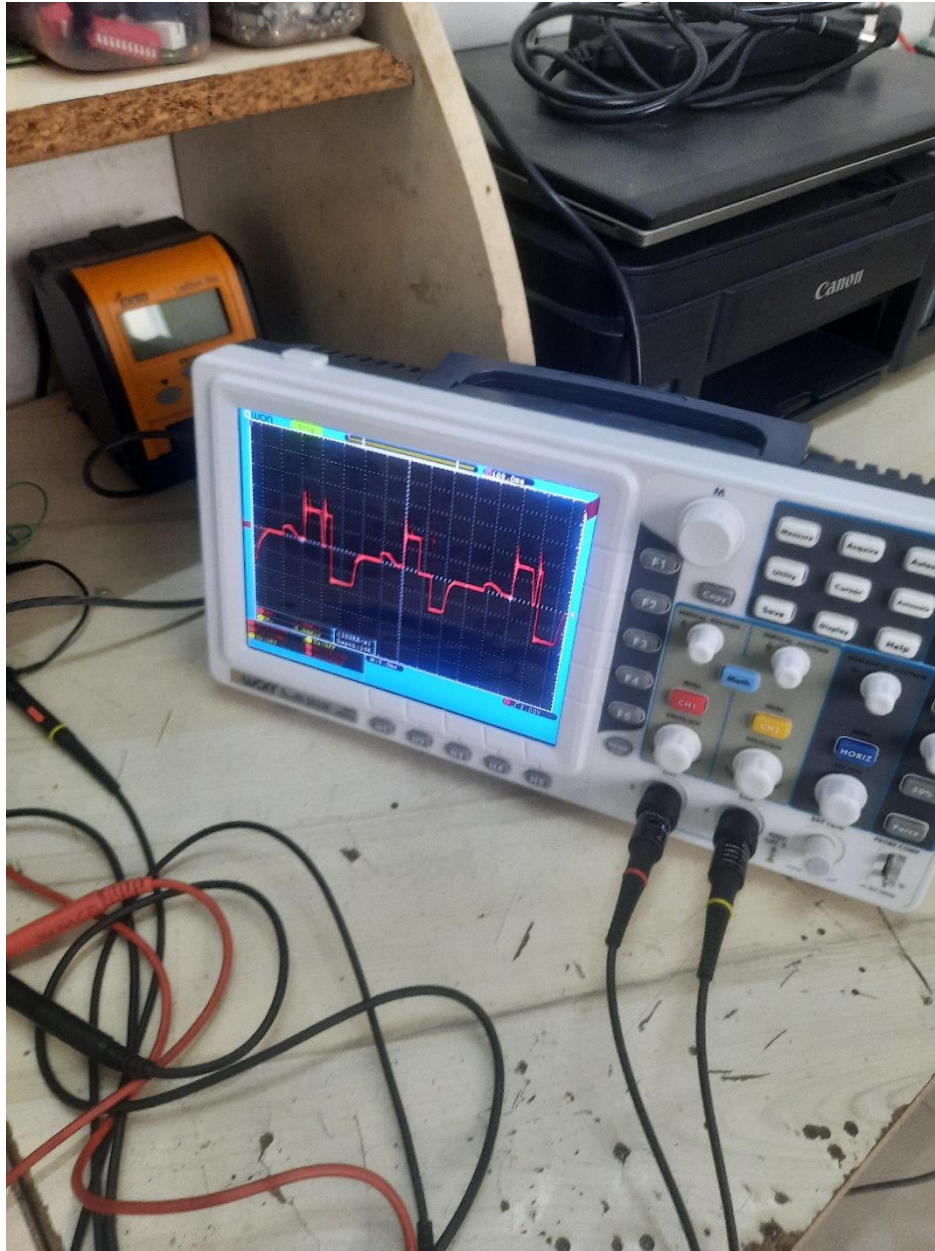


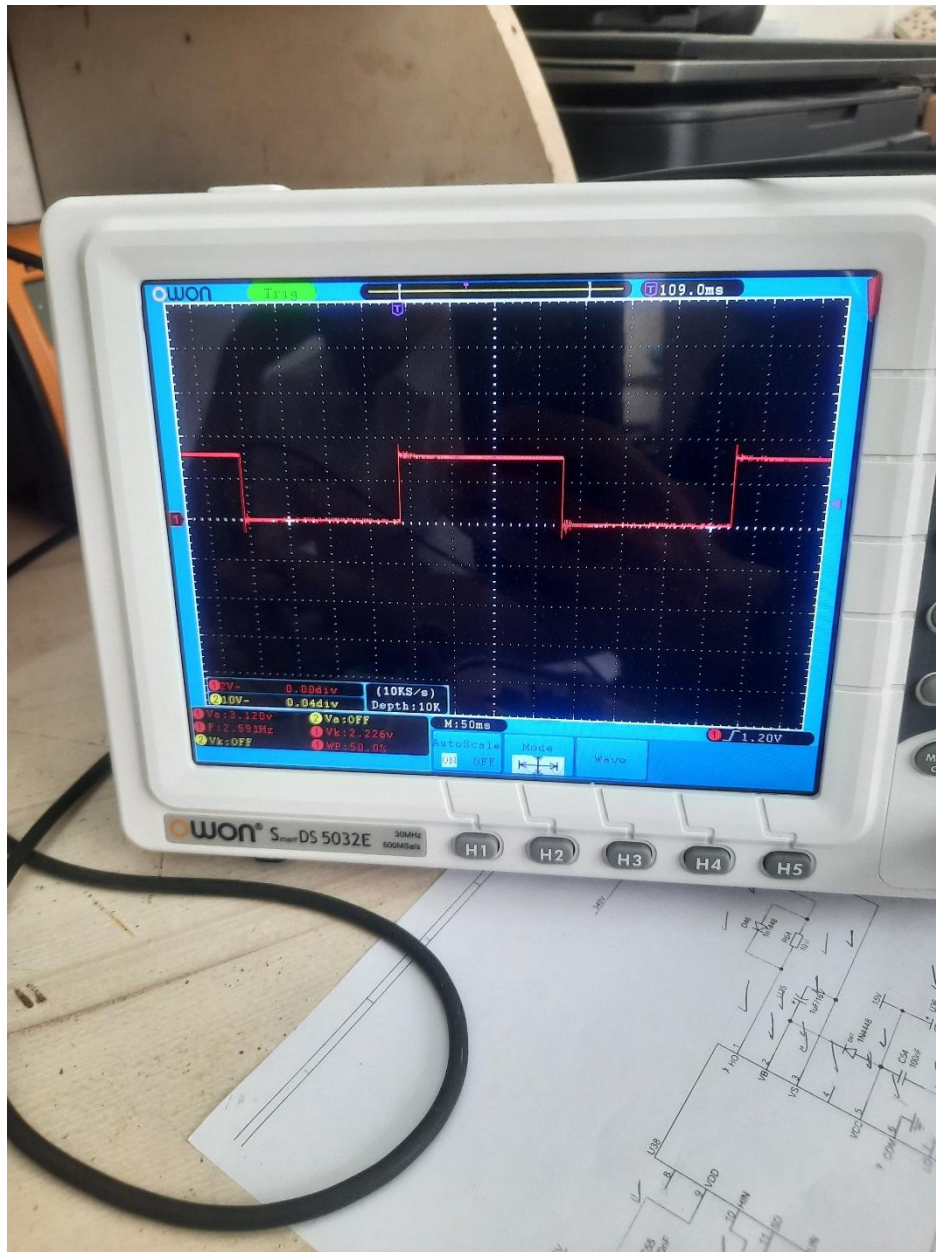

Figure 2 First working prototype with the vibrator



Figure 3 High voltage buck converter



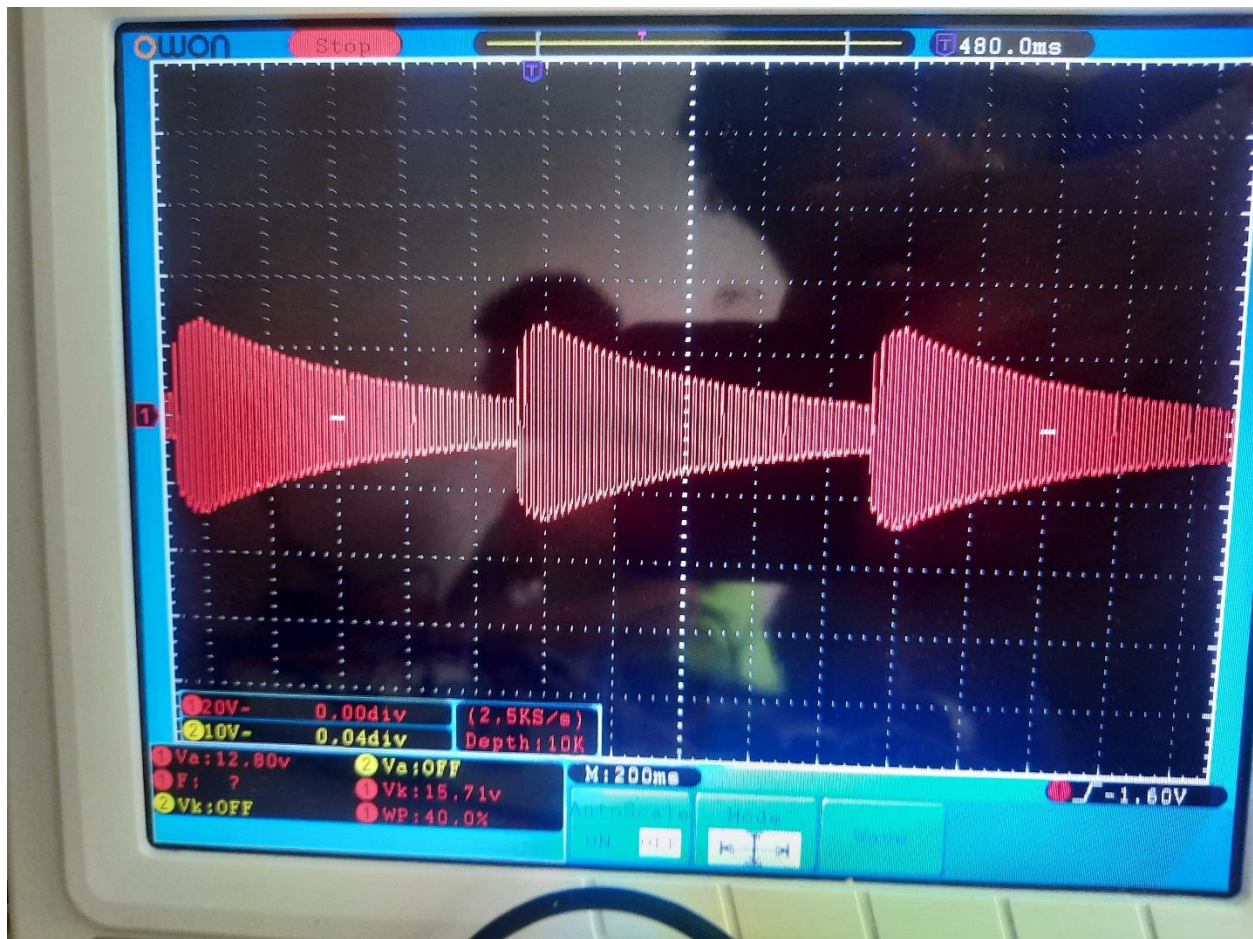


Figure 4 impedance mismatch between the VFD and the motor

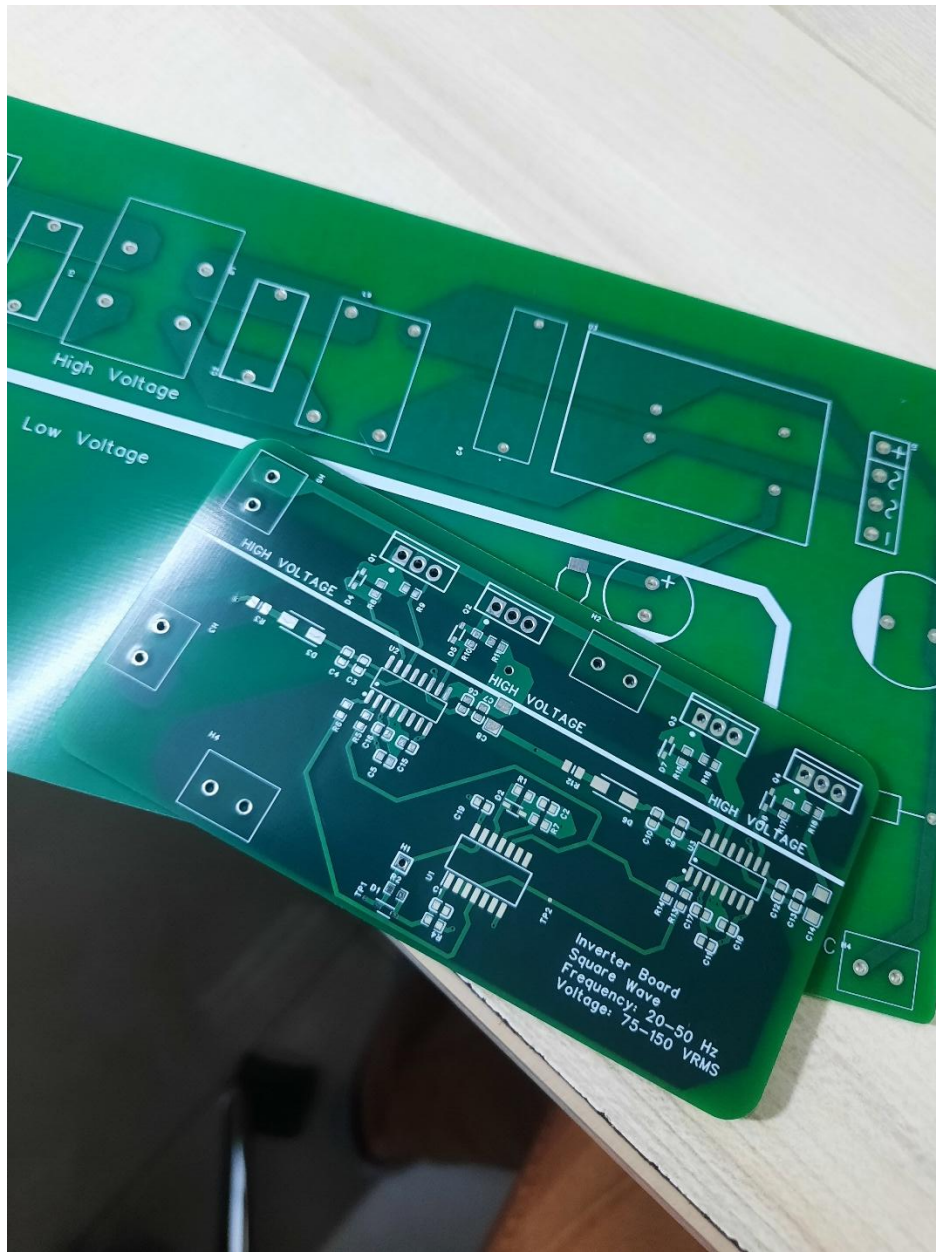


Figure 5 PCB shipment arrives

Buck Converter Stage

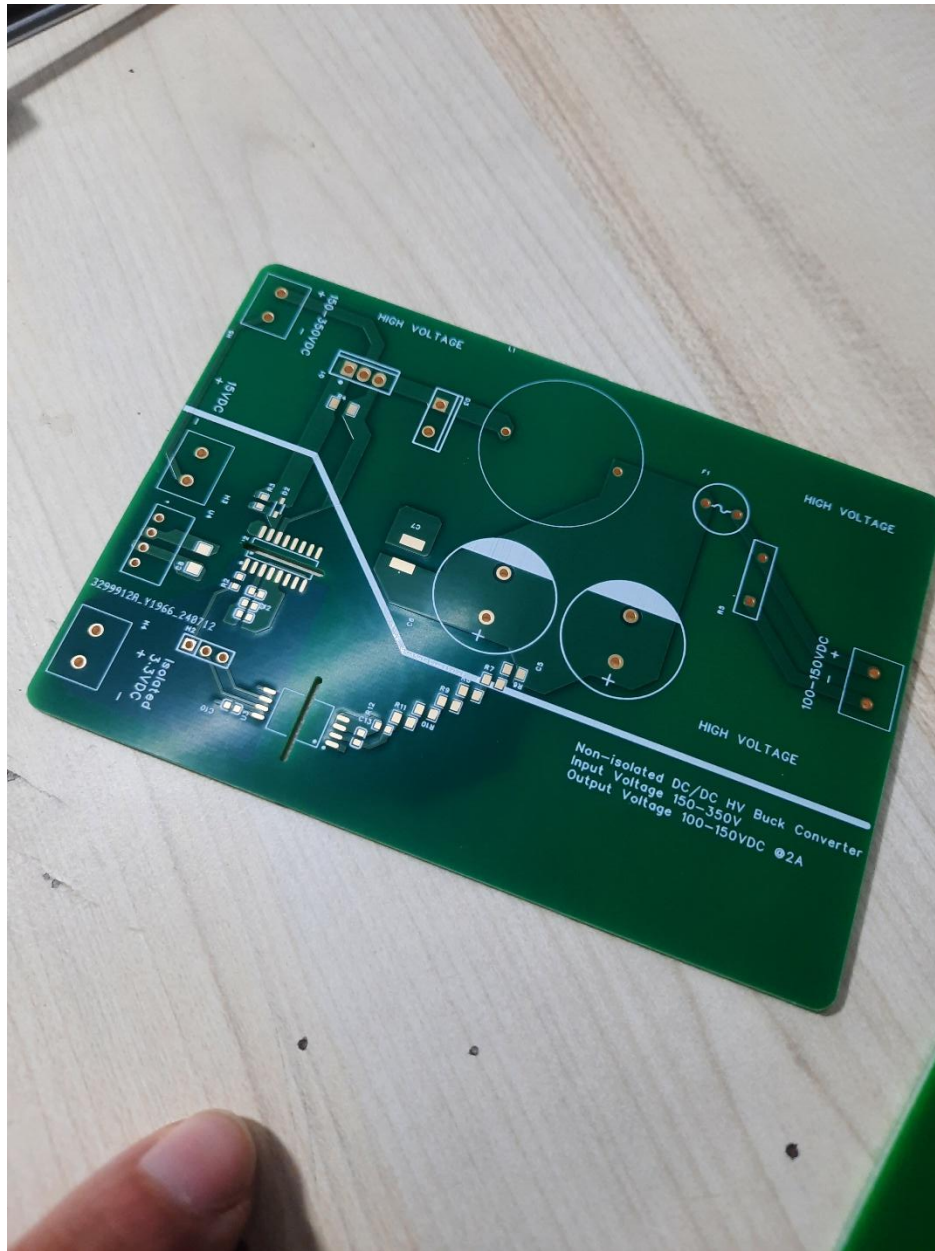


Figure 6 buck stage PCB



Figure 7 assembled AC-DC circuit with filters and power supply



Buck Converter Stage


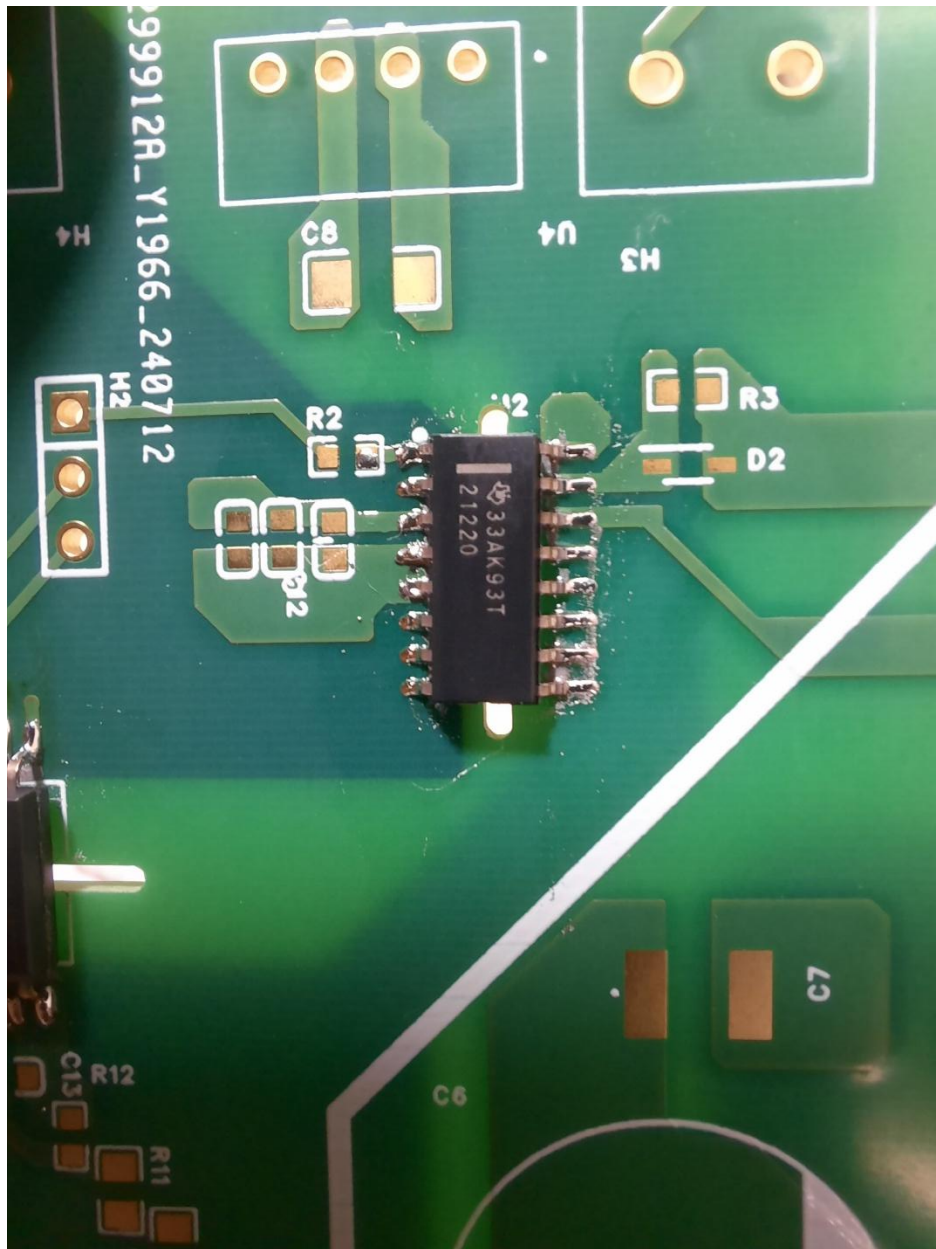



Figure 8 High Voltage Gate Driver IC

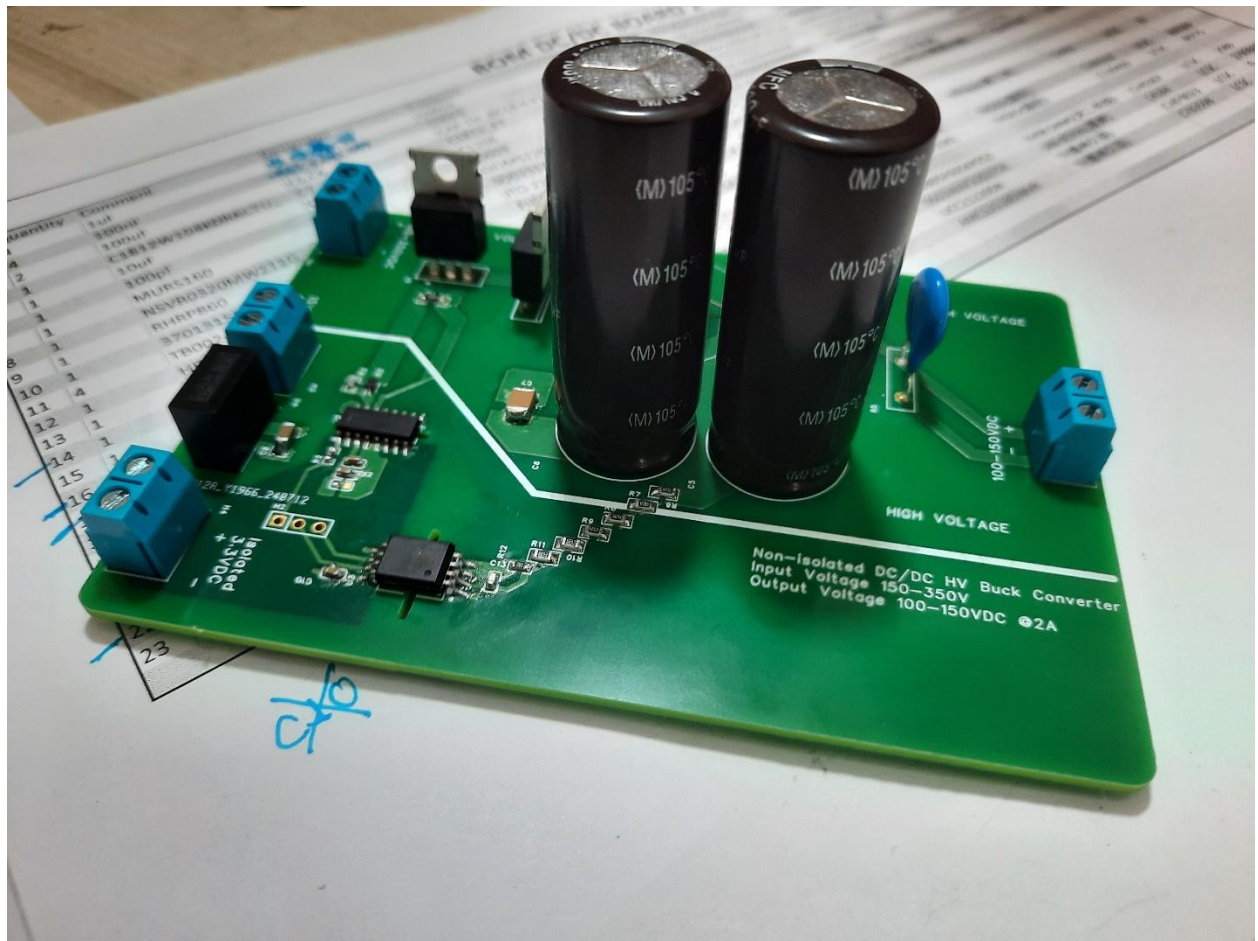

Figure 9 assembled buck converter and voltage sensing circuit for feedback



Assembled Inverter PCB

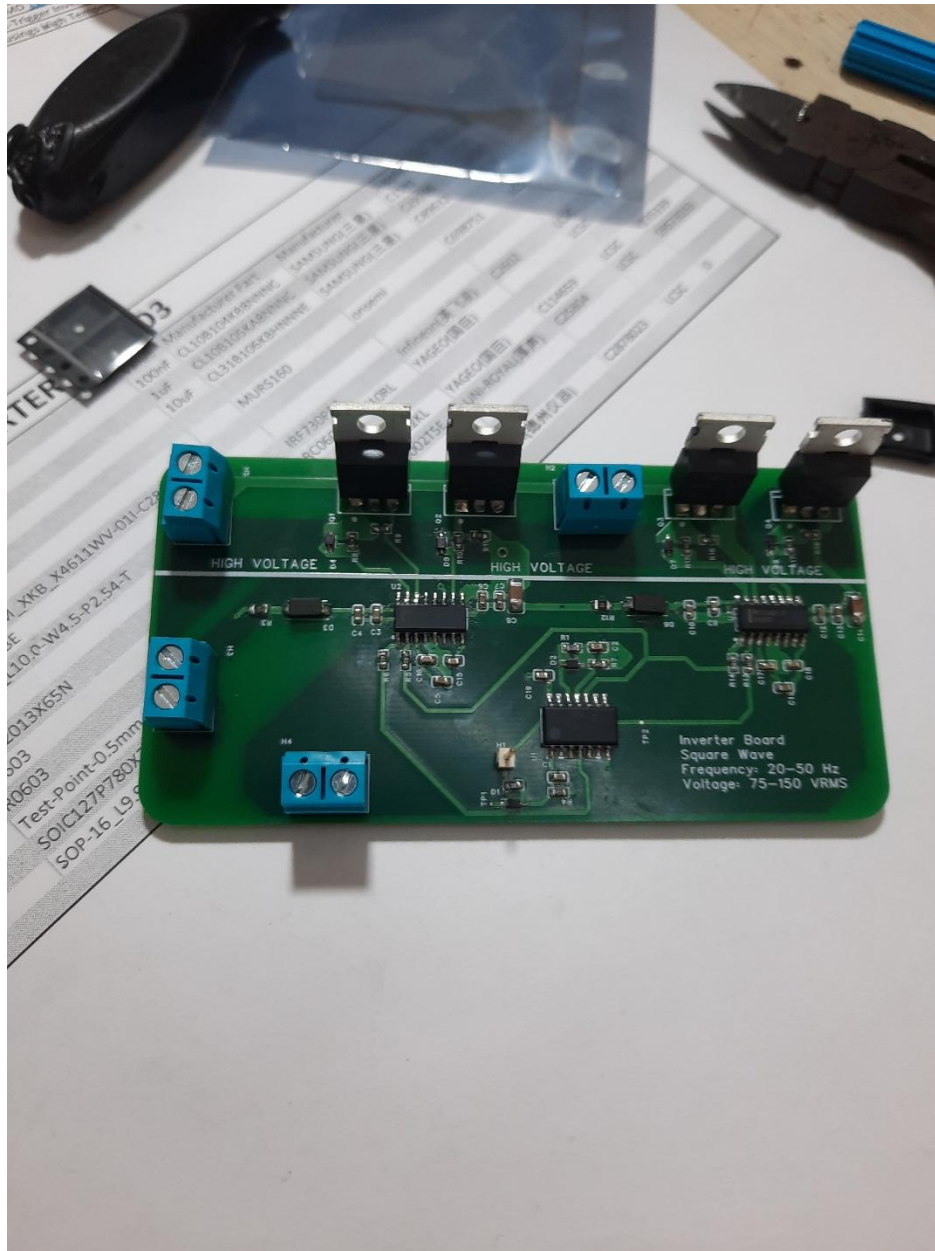



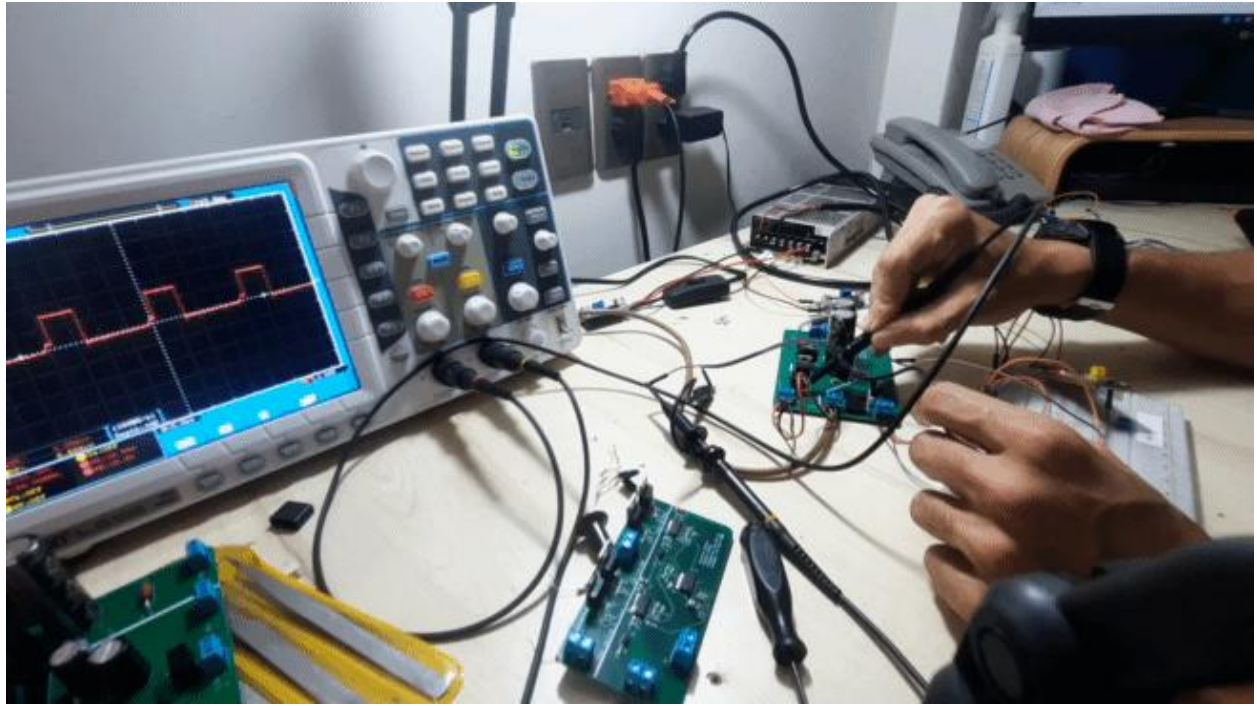


Figure 10 Testing signal integrity



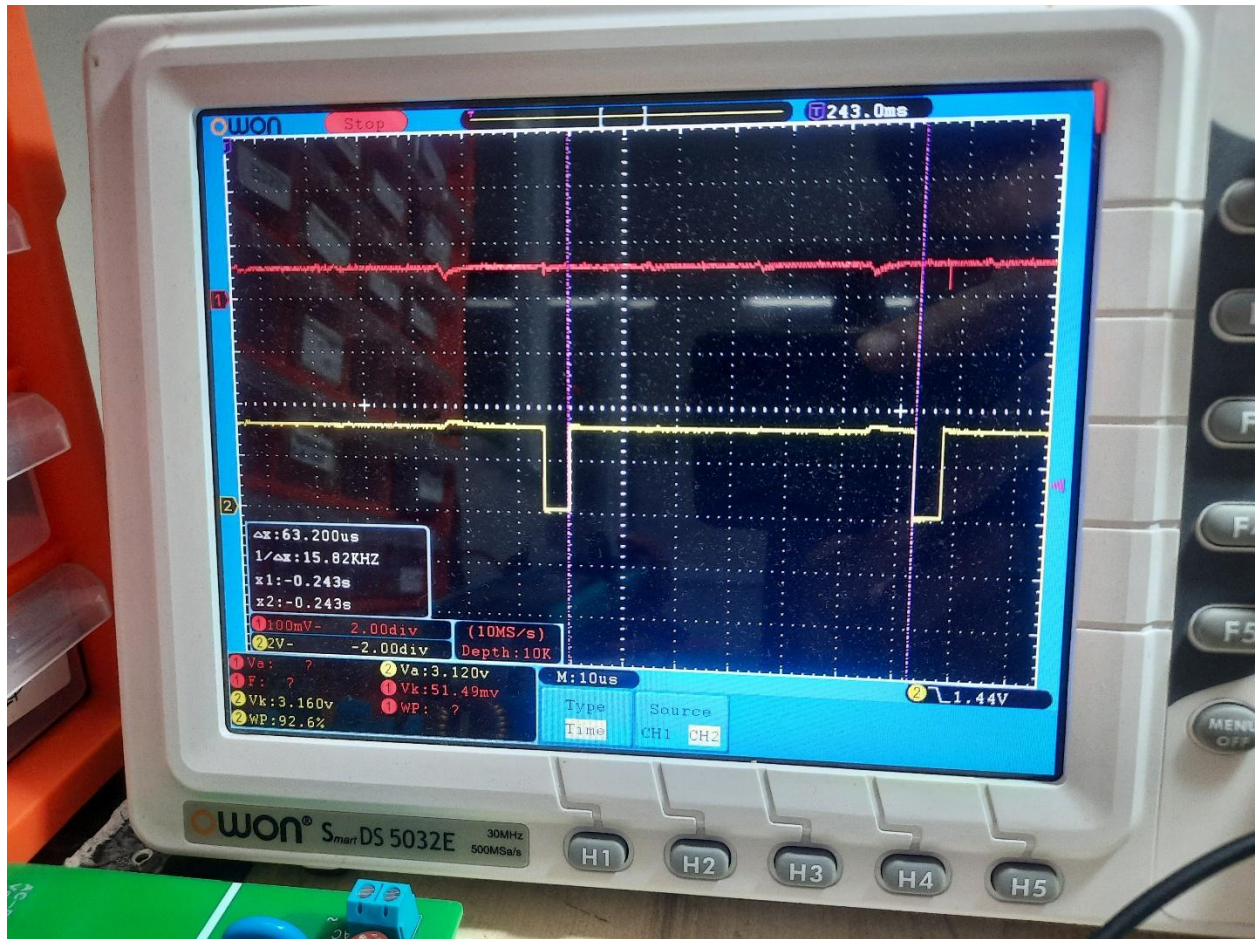


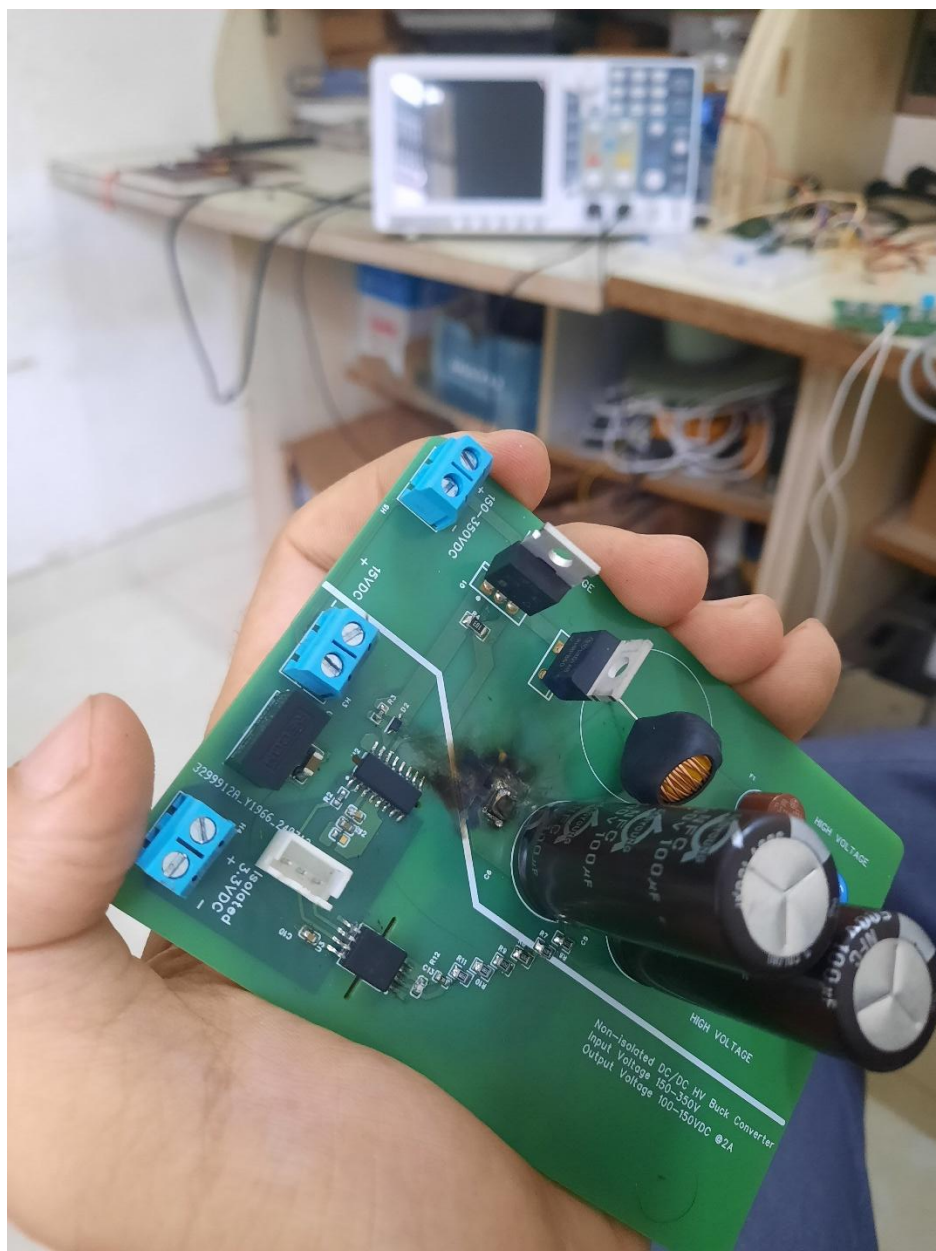

Figure 11 exploded capacitor: Unexpected Lesson in High-Voltage Creepage and Clearance

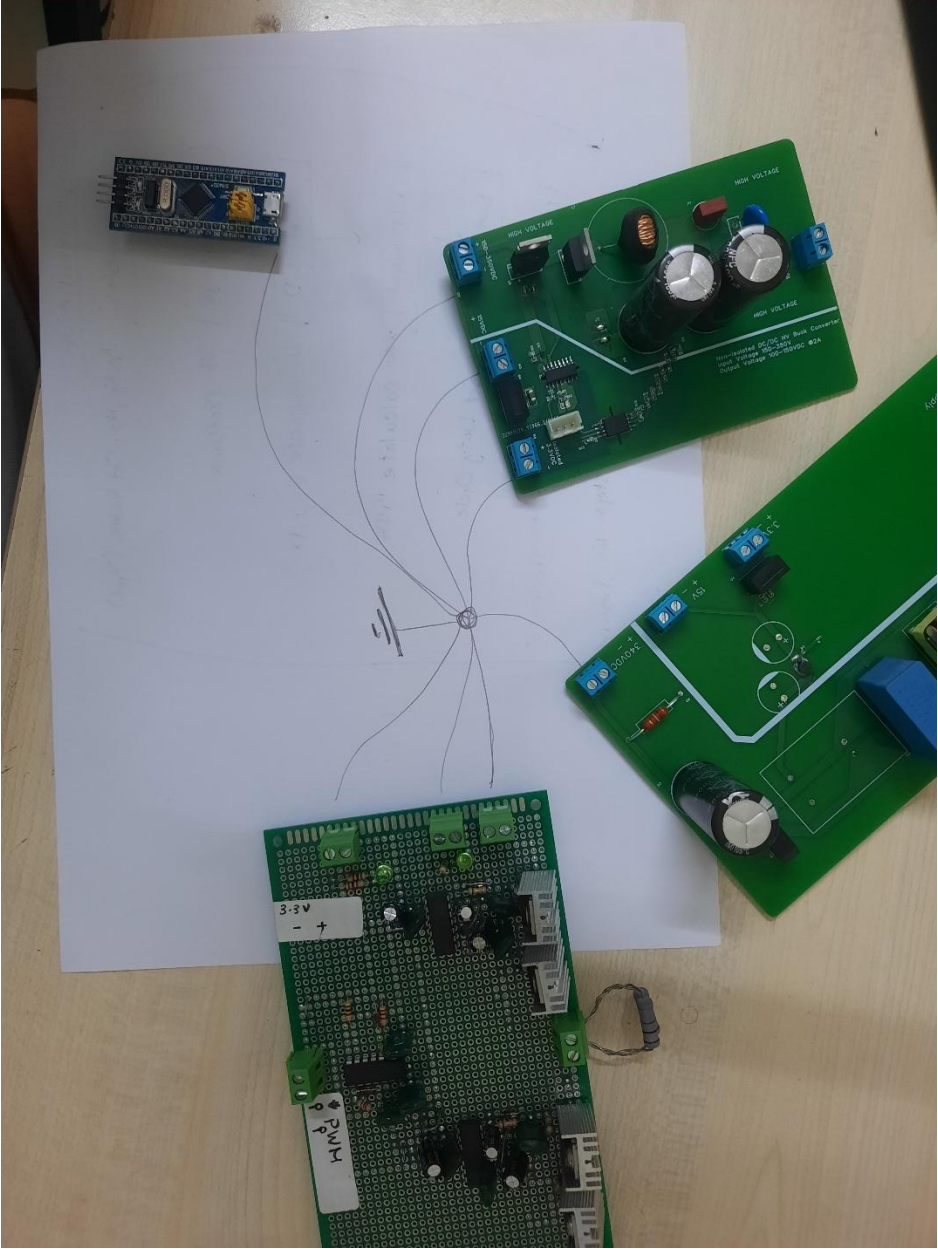



Simulation

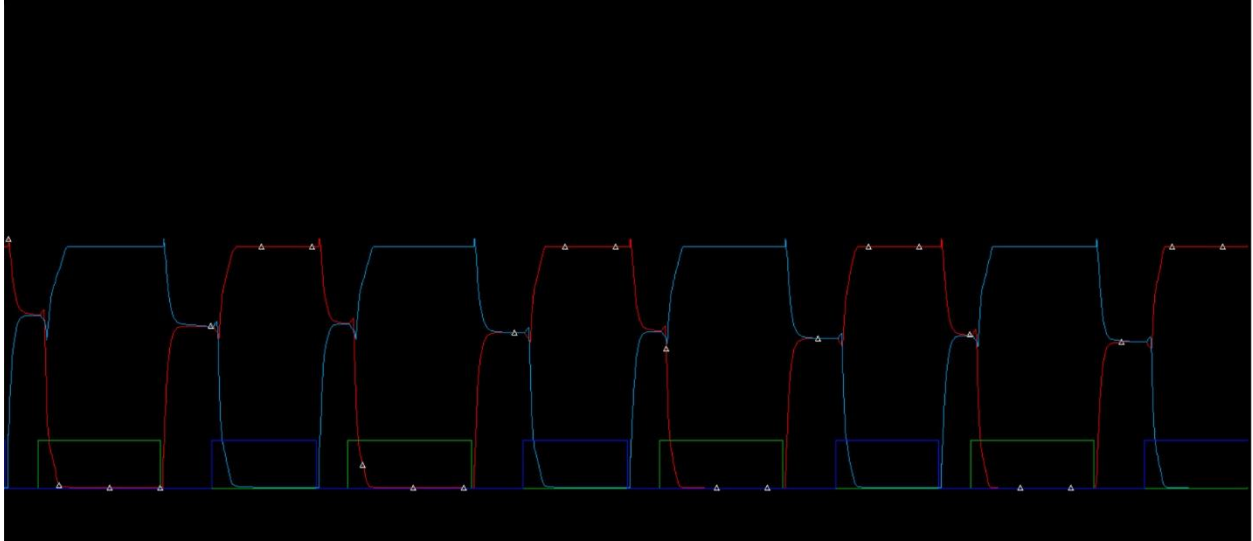


Figure 12 Deadtime circuit simulation on LTspice

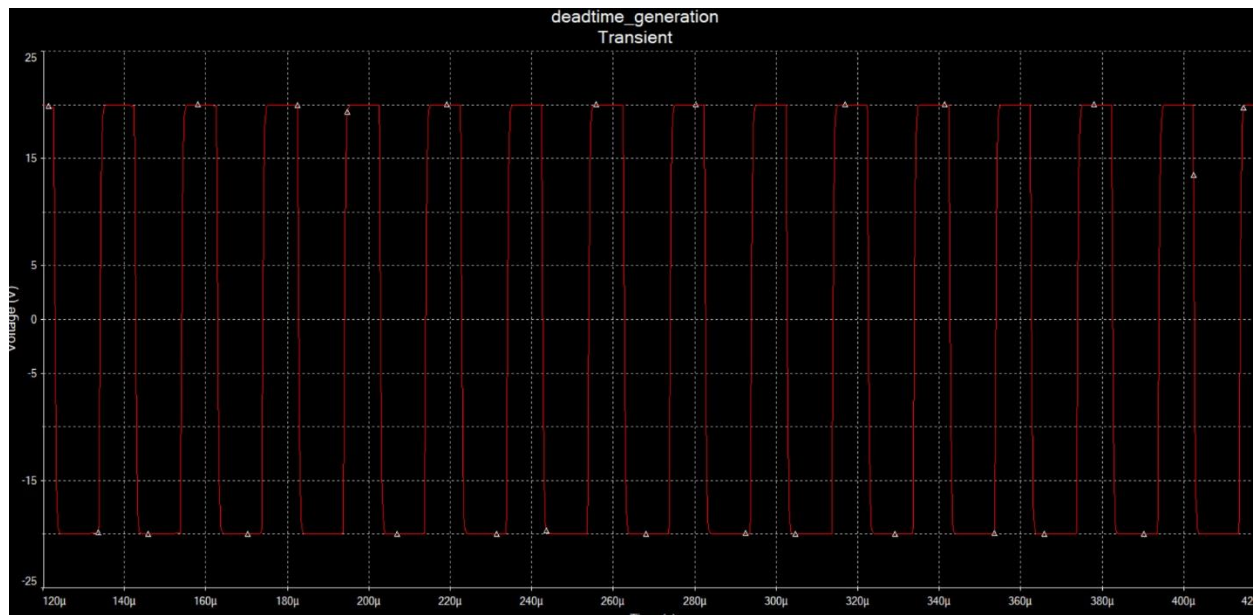


Figure 13 Deadtime generation circuit